Rx antennas at IV3PRK: the Test Oscillator

An improvement on the 1.843 KHz oscillator to test receiving antennas

by Pierluigi "Luis" Mansutti IV3PRK

After reading, many years ago, a good advice by Bob, W7LR, on the use of a 1.8432 KHz clock oscillator as a signal source for testing RX antennas on 160 meters, I built the simple circuit downloaded from the website of Dennis, K0CKD.

It is a very easy and cheap investment as the most expensive part of the circuit is the 9 volt battery! The price for one piece of these clock oscillators is 1.96 US\$ (Mouser catalogue part # 520-TCH184-X).

But after some tests with a small whip antenna I realized that something better was needed in order to get a useful test signal from at least one wavelength of distance, and so I added:

2 meter long antenna a ground connection

tuned output circuit.

9

The required inductance values are 16 μ H (in parallel with 470 pF) as a load and 3 μ H on the primary side. I got a T68-2 toroid (AL = 57), so 53 and 23 turns respectively are needed.

Clock oscillator

Zener

5 1

5

8

470 ohm





1N4733

March 2010

Luis IV3PRK

T68-2



10 KpF

<mark>3μΗ</mark> 23 t.

53 t. 470pF

BECS DE HALF SIZE (TTL/HCMOS) CLOCK OSCILLATORS

